

Assignment 7

Sharon Kachhi

January 2021

1 Boolean equation

$$F = \overline{P}Q + \overline{P}S + RQ + R\overline{S} \quad (1)$$

2 Logic Gate

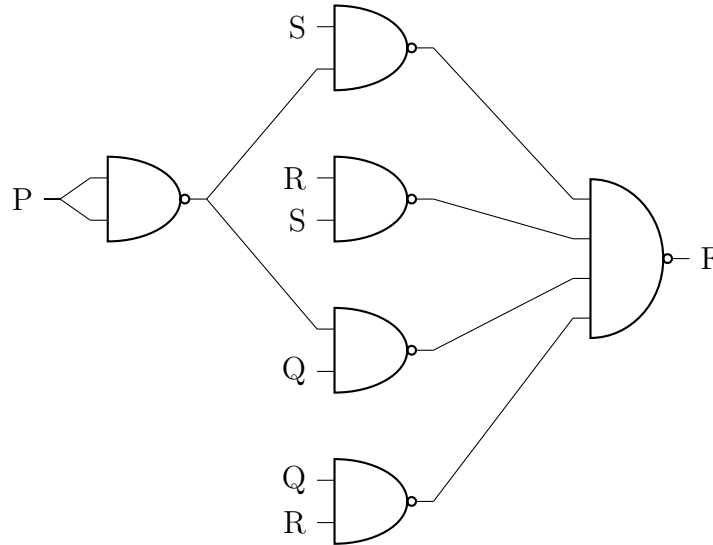


Figure 1: Logic Gate